

EE5123 VLSI Design Lab: Experiment 2

Saurav Kumar Pandey
System on Chip Design
IIT Palakkad
152502019@smail.iitpkd.ac.in

October 2025

Abstract

This report details the design and implementation of sequential logic circuits using Verilog, with a focus on Finite State Machines (FSMs). The experiment commences with the design of a 4-bit synchronous up/down counter. Building on this, a practical FSM-based traffic light controller is developed for a two-way intersection, initially managing red and green light cycles with countdown timers. The design is then enhanced to include a yellow warning light, creating a complete and realistic three-phase traffic control system.

1 Introduction

Finite State Machines (FSMs) are a fundamental concept in digital logic design, providing a powerful model for creating sequential circuits. This experiment focuses on the practical application of these concepts using the Verilog HDL to design and verify a 4-bit synchronous up/down counter and a complete traffic light controller FSM.

2 4-bit Up/Down Counter

2.1 Circuit Design

The counter's design features an adder/subtractor to generate the next count value, multiplexers controlled by 'mode', 'en', and 'reset' signals to select the correct input, and a D-type flip-flop to store the current count, synchronized to the clock.

 


Figure 1: Counter circuit diagram.

2.2 Verilog Implementation

```
module up_down_counter #(  
    parameter N = 4  
)  
(  
    input wire clk,  
    input wire reset,  
    input wire en,  
    input wire mode,  
    output reg [N-1:0] count  
)  
  
always @ (posedge clk) begin  
    if (reset) begin  
        count <= 0;  
    end else if (en) begin  
        if (mode) begin  
            count <= count + 1;  
        end else begin  
            count <= count - 1;  
        end  
    end  
end
```

```
endmodule
```

2.3 Verification

Testbench Code

```
'timescale 1ns/1ns
module up_down_counter_tb;
parameter N = 4;
reg clk, reset, en, mode;
wire [N-1:0] count;

up_down_counter #(N) uut (
    .clk(clk), .reset(reset), .en(en),
    .mode(mode), .count(count)
);

initial clk = 0;
always #5 clk = ~clk;

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(0, up_down_counter_tb);
    reset = 1; en = 0; mode = 0;
    #12 reset = 0; #5 en = 1;
    mode = 1; #40;
    mode = 0; #40;
    en = 0; #20;
    en = 1; mode = 1; #40;
    reset = 1; #10 reset = 0;
    #30; $finish;
end
endmodule
```

Simulation Output



Figure 2: Simulation waveform for the counter.

3 Traffic Light Controller FSM

3.1 Two-Phase Controller

The simple controller cycles between two states: HIGHWAY.GO and CROSSROAD.GO, with a counter determining the duration of each state.

Tuesday, 7 October 2025 9:50 PM

 


Figure 3: FSM diagram for two-phase controller.

Verilog Implementation

```
module traffic_light_controller #(
    parameter X = 6,
    parameter Y = 3
) (
    input wire      clk,
    input wire      reset,
    output reg     highway_green,
    output reg     highway_red,
    output reg     crossroad_green,
    output reg     crossroad_red,
    output reg [2:0] counter
);

localparam HIGHWAY_GO    = 2'b00;
localparam CROSSROAD_GO = 2'b01;

reg [1:0] current_state, next_state;

always @ (posedge clk or posedge reset) begin
    if (reset) begin
        current_state <= HIGHWAY_GO;
        counter       <= X;
    end else begin
        current_state <= next_state;
        if (counter == 0) begin
            if (current_state == HIGHWAY_GO)
                counter <= Y;
            else
                counter <= X;
        end else begin
            counter <= counter - 1;
        end
    end
end
```

```

        end
    end
end

always @(*) begin
    highway_green    = 1'b0;                               .highway_green(highway_green),
    highway_red     = 1'b1;                               .highway_red(highway_red),
    crossroad_green = 1'b0;                             .crossroad_green(crossroad_green),
    crossroad_red   = 1'b1;                             .crossroad_red(crossroad_red),
    next_state       = current_state;                  .counter(counter)
                                                                );
                                                                initial begin
                                                                clk = 0;
                                                                forever #5 clk = ~clk;
                                                                end
                                                                case (current_state)
                                                                HIGHWAY_GO: begin
                                                                highway_green = 1'b1;           initial begin
                                                                highway_red   = 1'b0;           reset = 1;
                                                                if (counter == 0) begin         #25;
                                                                next_state = CROSSROAD_GO;    reset = 0;
                                                                end                           #300;
                                                                $finish;                      end
                                                                end                           end
                                                                end
                                                                CROSSROAD_GO: begin
                                                                crossroad_green = 1'b1;         initial begin
                                                                crossroad_red   = 1'b0;         $dumpfile("traffic.vcd");
                                                                if (counter == 0) begin         $dumpvars(0, traffic_light_controller_tb);
                                                                next_state = HIGHWAY_GO;      end
                                                                end                           endmodule
                                                                end
                                                                endcase
                                                                end
endmodule

```

Testbench

```

'timescale 1ns / 1ps

module traffic_light_controller_tb;

reg clk;
reg reset;

wire highway_green;
wire highway_red;
wire crossroad_green;
wire crossroad_red;
wire [2:0] counter;

traffic_light_controller #(
    .X(6),
    .Y(3)
) dut (
    .clk(clk),
    .reset(reset),

```



Figure 4: Simulation waveform for the two-phase traffic controller.

3.2 Three-Phase Controller

The design was modified to include a yellow light. This adds yellow warning states, creating a four-state machine that provides a safe transition time for traffic.

Verilog Implementation

```

module tlc_3phase #(
    parameter H_GREEN_T = 6,
    parameter H_YELLOW_T = 2,
    parameter C_GREEN_T = 4,
    parameter C_YELLOW_T = 2
)()

```

 


Figure 5: FSM diagram for the three-phase controller.

```

S_HY: if(counter==0) next_state = S_CG;
      else next_state = S_HY;
S_CG: if(counter==0) next_state = S_CY;
      else next_state = S_CG;
S_CY: if(counter==0) next_state = S_HG;
      else next_state = S_CY;
endcase
end

always @(*) begin
    h_green=0; h_yellow=0; h_red=1;
    c_green=0; c_yellow=0; c_red=1;
    case(state)
        S_HG: {h_green,h_red}={1'b1,1'b0};
        S_HY: {h_yellow,h_red}={1'b1,1'b0};
        S_CG: {c_green,c_red}={1'b1,1'b0};
        S_CY: {c_yellow,c_red}={1'b1,1'b0};
    endcase
end
endmodule

```

```

input wire clk, reset,
output reg h_green, h_yellow, h_red,
output reg c_green, c_yellow, c_red
);
localparam S_HG = 2'b00, S_HY = 2'b01,
          S_CG = 2'b10, S_CY = 2'b11;
reg [1:0] state, next_state;           'timescale 1ns / 1ps
reg [2:0] counter;                   module tlc_3phase_tb;
                                      reg clk, reset;
always @(posedge clk or posedge reset) begin
    wire h_green, h_yellow, h_red;
    wire c_green, c_yellow, c_red;
    if(reset) state <= S_HG;
    else state <= next_state;
end
always @(posedge clk or posedge reset) begin
    if(reset) counter <= H_GREEN_T;
    else if (counter == 0)
        case(next_state)
            S_HG: counter <= H_GREEN_T;
            S_HY: counter <= H_YELLOW_T; initial begin
            S_CG: counter <= C_GREEN_T;     clk = 0;
            S_CY: counter <= C_YELLOW_T;   forever #5 clk = ~clk;
        endcase
    end
    else counter <= counter - 1;
end
initial begin
    reset = 1; #15;
    reset = 0; #300;
    $finish;
end
always @(*) begin
    case(state)
        S_HG: if(counter==0) next_state = S_HY;
        else next_state = S_HG; endmodule

```



Figure 6: Simulation waveform for the three-phase traffic controller.

Simulation Output

4 Conclusion

This experiment successfully demonstrated the design of sequential circuits in Verilog. A synchronous 4-bit up/down counter was created and verified, and an FSM was used to model and implement a realistic three-phase traffic light controller, reinforcing the principles of state-based design.